
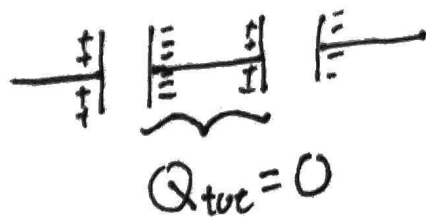


DC Circuits II - Capacitors


Resistors

Capacitors


Conservation of charge

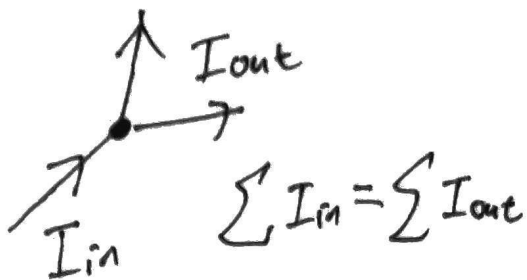

Electric potential is well defined

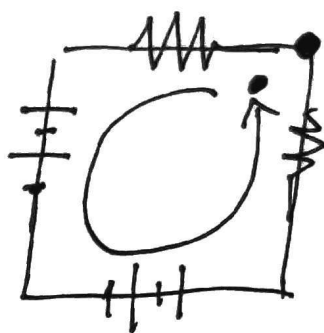


$$\sum_{loop} \Delta V = 0$$

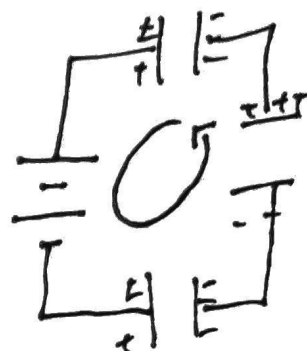

Series:



\equiv

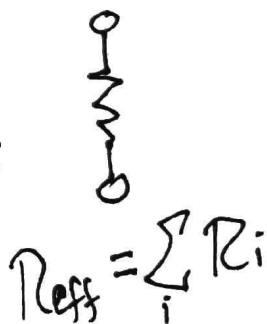

$$R_{eff} = \sum_i R_i$$




\approx



$$C_{eff}^{-1} = \sum C_i^{-1}$$

$$(C = \epsilon_0 \frac{A}{d})$$


Parallel:

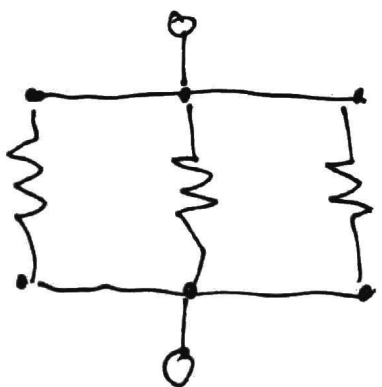


\equiv



$$R_{eff}^{-1} = \sum_i R_i^{-1}$$

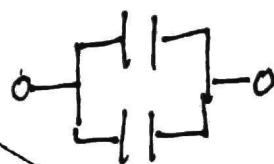

$$C_{eff} = \sum C_i$$

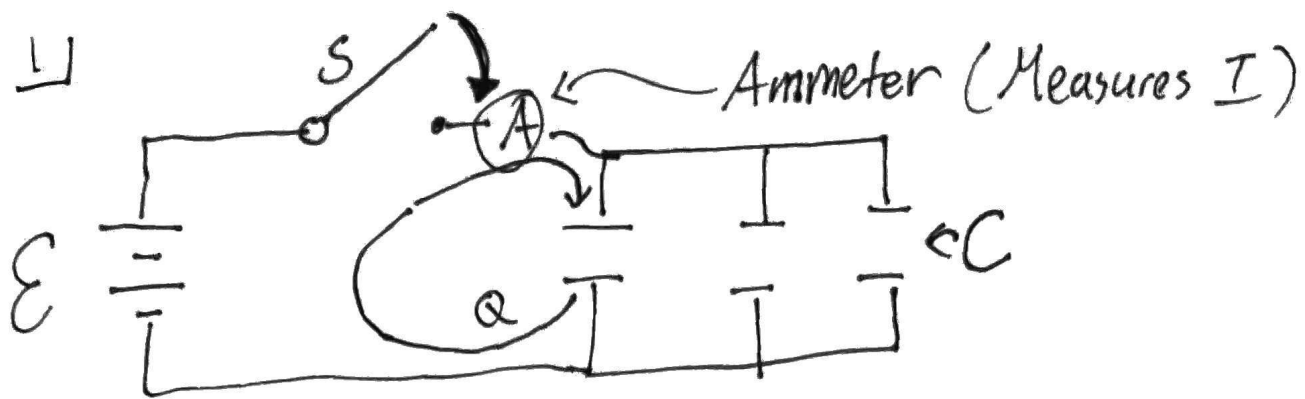


Initially, S is open, and capacitors are uncharged.

Q: How much Q_{tot} flows through A when switch is closed?

Two approaches:

(i) Because they are in parallel:

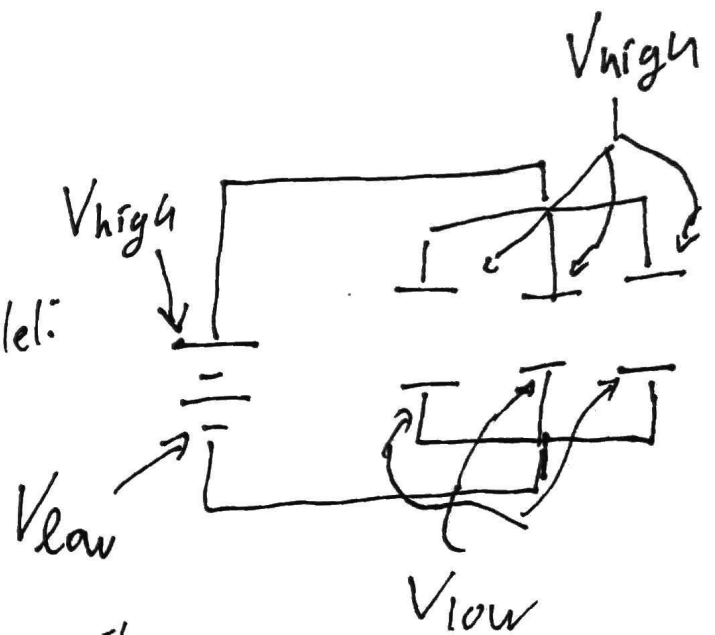

$\Rightarrow \Delta V$ for each capacitor is the same: $\Delta V = V_{high} - V_{low} = \mathcal{E}$

Each capacitor ends up w/ $Q = C \cdot \Delta V = C\mathcal{E}$

$$Q_{tot} = Q + Q + Q = 3C\mathcal{E}$$

$$\Delta V_1 = Q_1' / C_1, \quad \Delta V_2 = Q_2' / C_2$$

$$\hookrightarrow \frac{Q_1'}{C_1} = \frac{Q_2'}{C_2} \Rightarrow \frac{Q_1'}{Q_2'} = \frac{C_1}{C_2} = \frac{1}{3}$$

$$\boxed{Q_2' = 3Q_1'}$$


$$Q_1' + Q_2' = 12 \mu\text{C}$$

$$Q_1' + 3Q_1' = 4Q_1' = 12 \mu\text{C}$$



$$\boxed{Q_1' = 3 \mu\text{C}} \Rightarrow \boxed{Q_2' = 9 \mu\text{C}}$$

$$\Delta V = \frac{Q_1'}{C_1} = \frac{3 \mu\text{C}}{1 \mu\text{F}} = 3 \text{V}$$
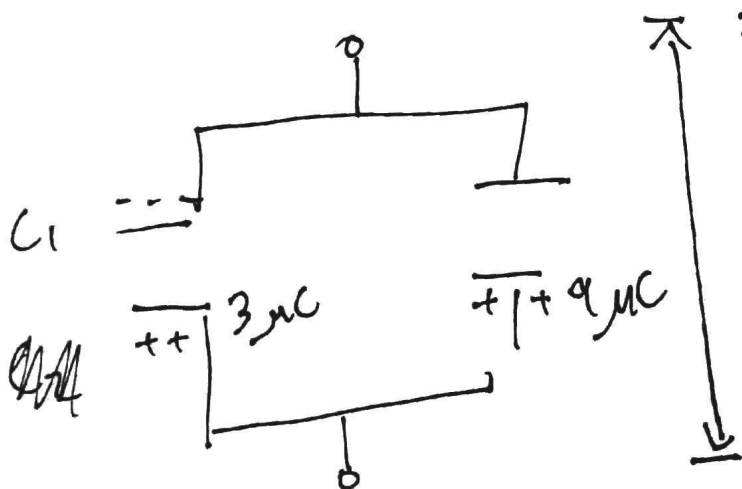
$$= \frac{Q_2'}{C_2} = \frac{9 \mu\text{C}}{3 \mu\text{F}} = 3 \text{V}$$




(i) Effective capacitor \approx (Parallel) $C_{\text{eff}} = C + C + C = 3C$
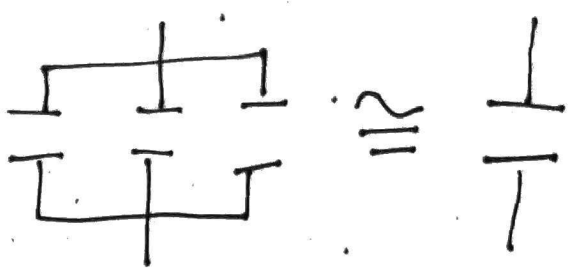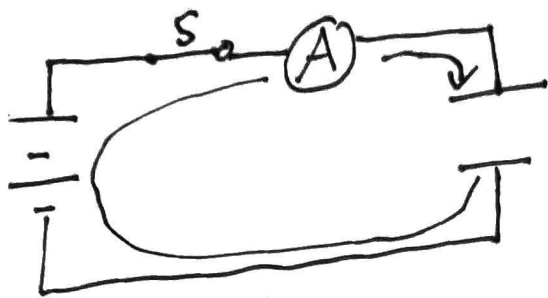
$$\Delta V = \mathcal{E}$$

$$Q_{\text{total}} = (3C) \cdot \mathcal{E} \quad \checkmark$$

Why does the C get charged?

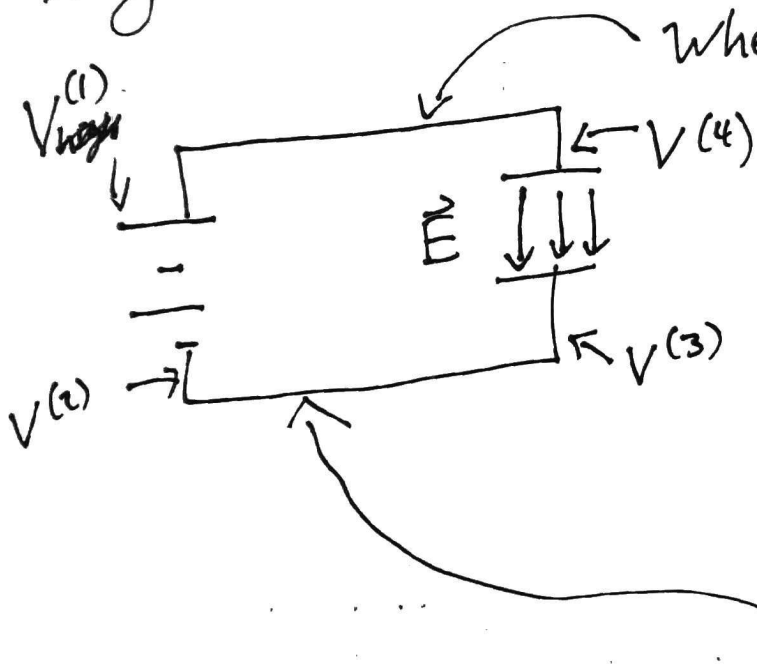

When I close the switch,

Connect top of battery, to top of capacitor w/ wire.

$$\Rightarrow V^{(1)} = V^{(4)}$$


$$V^{(2)} = V^{(3)}$$

$$\Delta V_{\text{capacitor}} \equiv V^{(4)} - V^{(3)} = V^{(1)} - V^{(2)}$$

$$\equiv \Delta V_{\text{battery}} = \mathcal{E} \neq 0$$

Charge $Q = C \cdot \Delta V$

2]

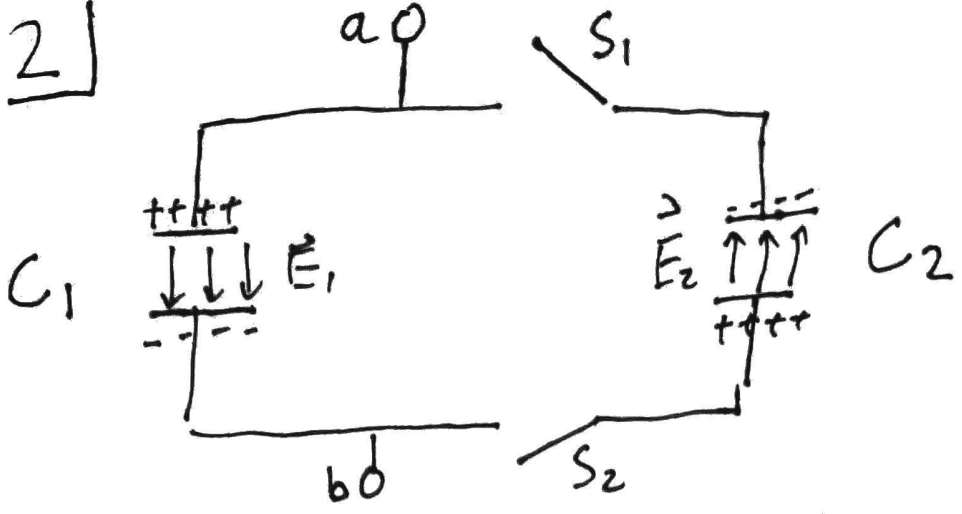

(\vec{E} points from + to - charges, from $V_{high} \rightarrow V_{low}$)



Initially, I have two charged capacitors,
 s.t. $|\Delta V_1| = |\Delta V_2| = 6\text{ V}$

$C_1 = 1\ \mu\text{F}$, $C_2 = 3\ \mu\text{F}$

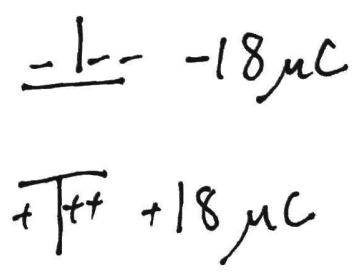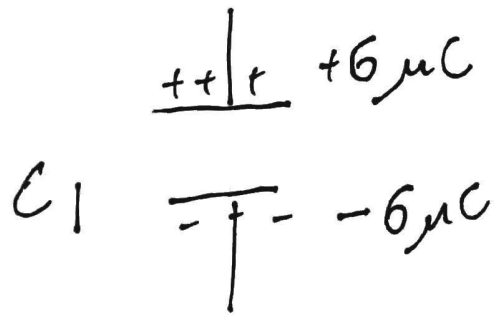(d) Initial charges?

$Q_1 = C_1 \cdot \Delta V_1$
 $= 1\ \mu\text{F} \cdot 6\text{ V} = 6\ \mu\text{C}$


$Q_2 = C_2 \cdot \Delta V_2 = 18\ \mu\text{C}$



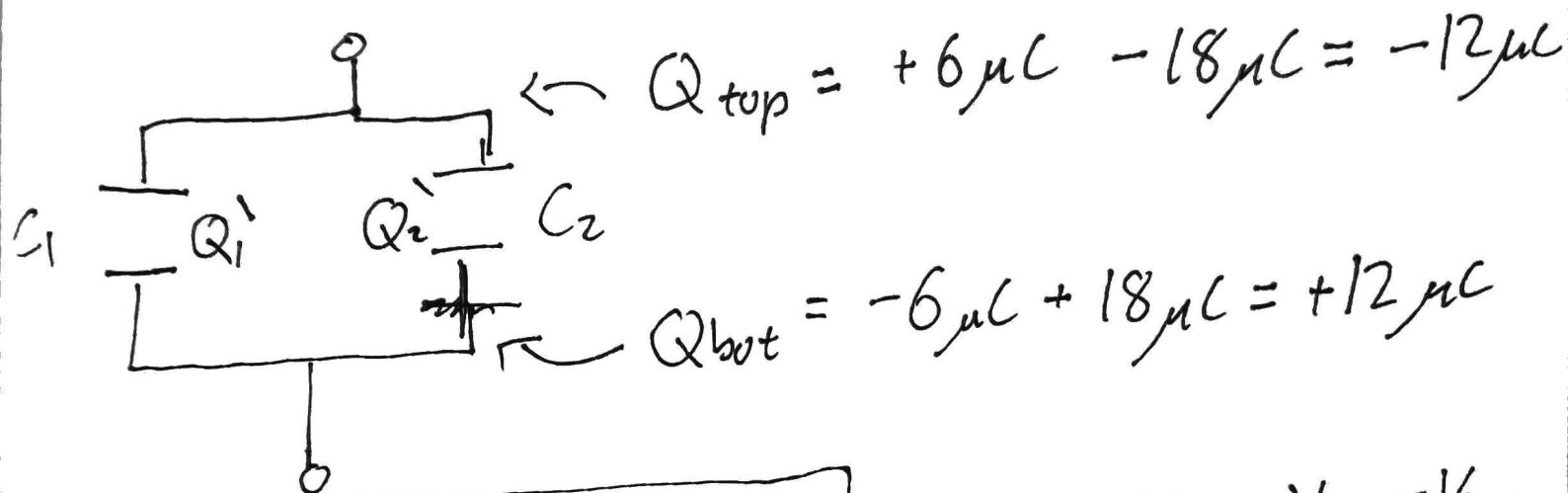(b) What happens when switches are closed?

(If no external voltage applied)


↳ total charges on top & bottom halves each conserved



$$Q_1' + Q_2' = 12 \mu C$$



$$\Delta V_1 = \Delta V_2 = V_{top} - V_{bot}$$

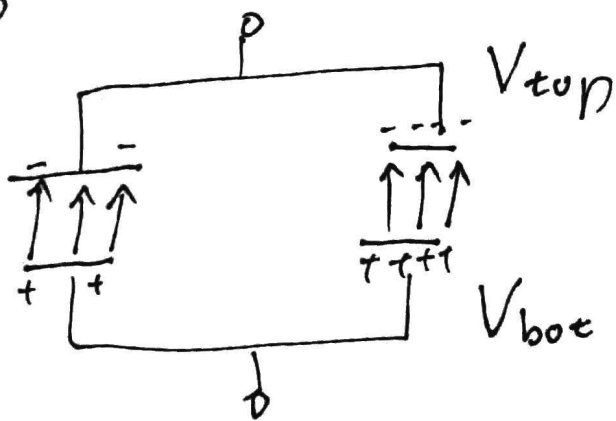Each capacitor is charged in same direction:
Two are



\vec{E} in each C
 points in same
 direction (up)

(ii) Effective capacitor

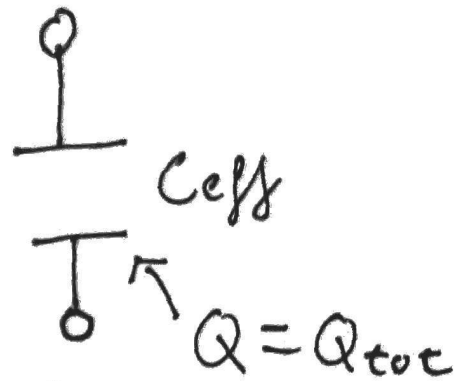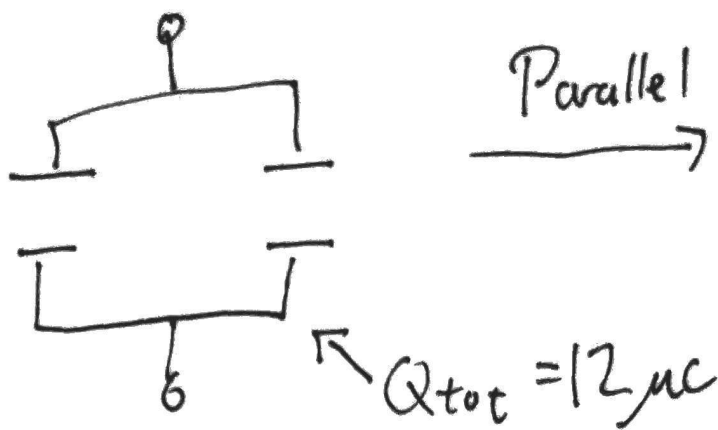


$$C_{\text{eff}} = 3 \mu\text{F} + 1 \mu\text{F} = 4 \mu\text{F}$$


$$\Delta V = \frac{Q_{\text{tot}}}{C_{\text{eff}}} = \frac{12 \mu\text{C}}{4 \mu\text{F}} = 3 \text{ V}$$

$$\Rightarrow Q_1 = C_1 \cdot \Delta V = 1 \mu\text{F} \cdot 3 \text{ V} = 3 \mu\text{C}$$
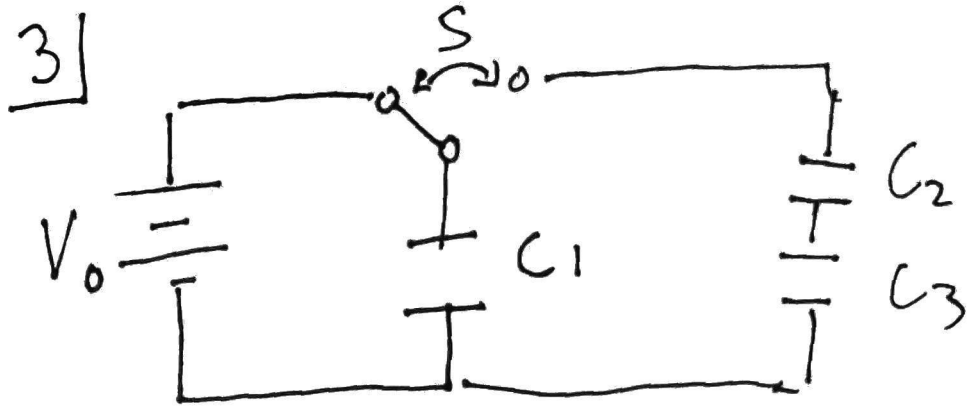
$$Q_2 = C_2 \cdot \Delta V = 3 \mu\text{F} \cdot 3 \text{ V} = 9 \mu\text{C}$$




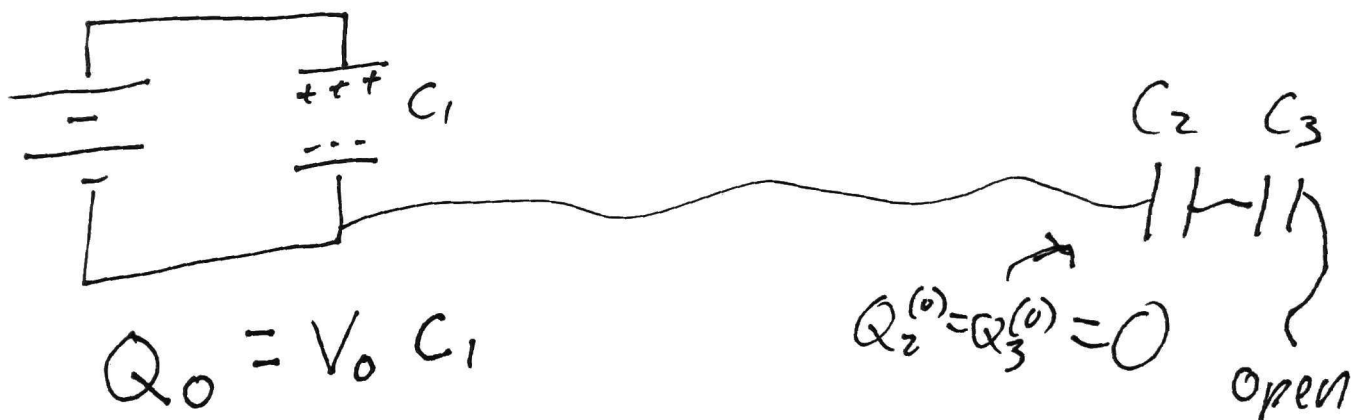Initially, switch is to the left,
and only C_1 is charged:




Throw switch to right

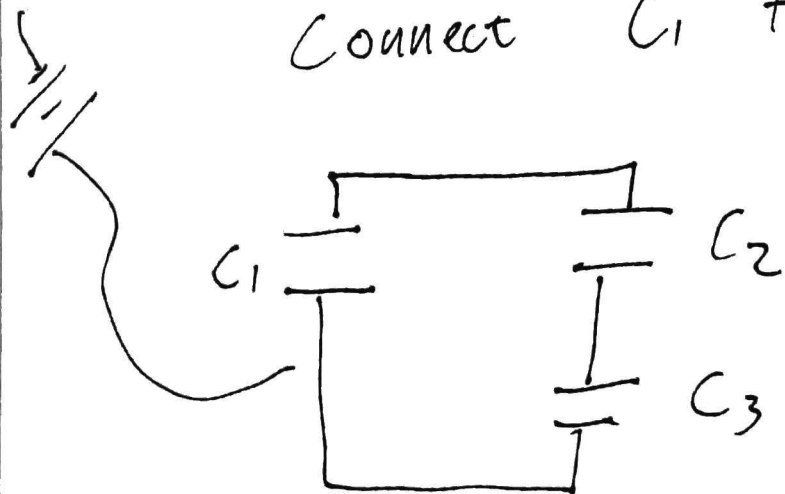⇒ Disconnect C_1 from battery,
Connect C_1 to C_2, C_3



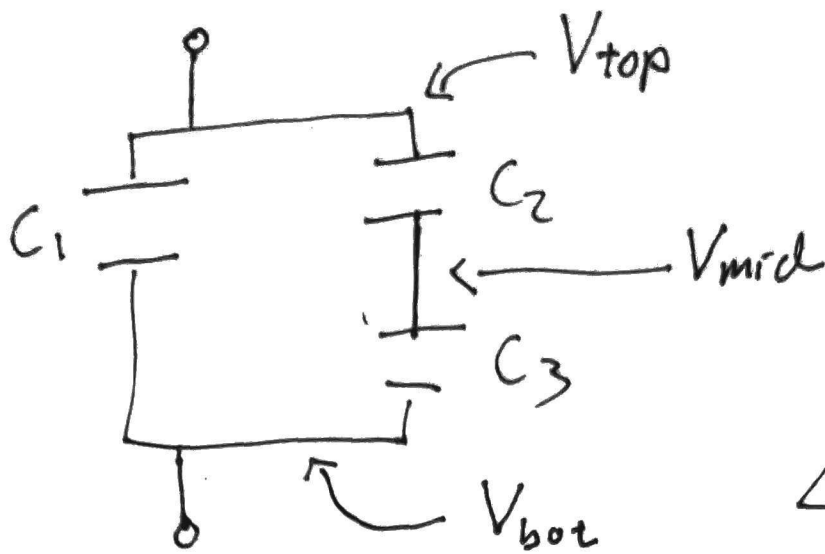How does
 Q_0 redistribute
onto other capacitors?




$$\Delta V_1 = V_{top} - V_{bot}$$

$$\Delta V_2 = V_{top} - V_{mid}$$

$$\Delta V_3 = V_{mid} - V_{bot}$$

$$\Delta V_1 = \Delta V_2 + \Delta V_3$$

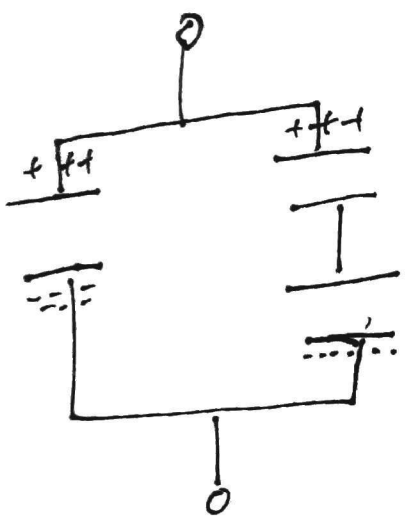↳ C_1 is in parallel w/ C_2 & C_3
 C_2 & C_3 are in series.



$$C_{23} = \left(\frac{1}{C_2} + \frac{1}{C_3} \right)^{-1}$$

$$C_{eff} = C_1 + C_{23}$$

$$Q_{tot} = Q_0$$

Because the $\pm Q_0$ can only move along wires (can't hop across)

$$Q_2 = Q_0 - Q_1 = Q_0 \left(1 - \frac{C_1}{C_1 + C_{23}} \right)$$

$$= Q_0 \frac{C_{23}}{C_1 + C_{23}}$$

$$Q_3 = Q_0 - Q_1 = Q_0 \frac{C_{23}}{C_1 + C_{23}}$$

Voltage drops:

$$\Delta V_2 = Q_2 / C_2 = Q_0 \frac{C_{23} / C_2}{C_1 + C_{23}}$$


$$\Delta V_3 = Q_3 / C_3 = Q_0 \frac{C_{23} / C_3}{C_1 + C_{23}}$$

(Check: $\Delta V_2 + \Delta V_3 = \Delta V_1$)

($C_2 > C_3 \Rightarrow \Delta V_2 < \Delta V_3$, $\Delta V_2 = \frac{C_3}{C_2} \cdot \Delta V_3$)

Found $Q_2 = Q_3$.

Can we explain this?

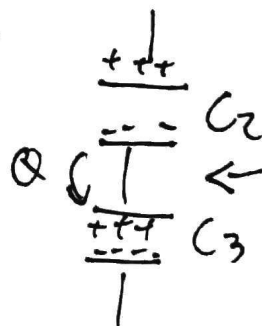


Middle region initially uncharged.

$$0 = -Q_2 + Q_3$$

$$\Rightarrow \boxed{Q_2 = Q_3}$$

$$\Delta V_{\text{eff}} = \frac{Q_{\text{tot}}}{C_{\text{eff}}} = \frac{Q_0}{C_1 + C_{23}} = \frac{V_0 C_1}{C_1 + C_{23}}$$

$$= V_0 \cdot \frac{C_1}{C_1 + C_{23}}$$

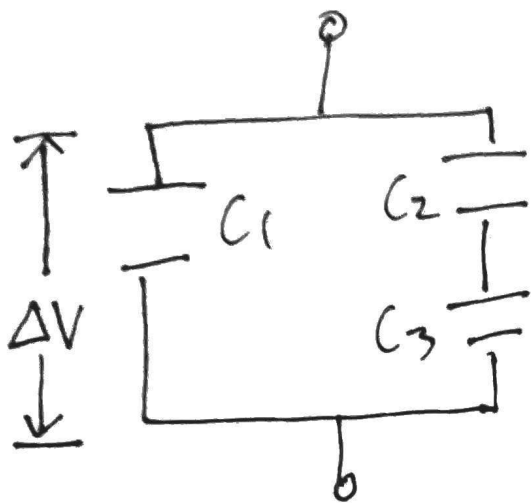

$$\Delta V_1 = \Delta V_{\text{eff}}$$

$$= V_0 \cdot \frac{C_1}{C_1 + C_{23}}$$

$$\leq 1$$

$$Q_1 = C_1 \cdot \Delta V_1$$

$$= (C_1 V_0) \cdot \frac{C_1}{C_1 + C_{23}}$$

$$= Q_0 \cdot \frac{C_1}{C_1 + C_{23}}$$

Charge

conservation: $Q_0 = Q_1 + Q_2$ (+ charges on top)

$Q_0 = Q_1 + Q_3$ (- charges on bottom)